

Preset & Clear in SR FlipFlop

They are asynchronous i/p i.e. they do not require any clock. They can be operated in any application. In many applications, it is desired that before starting any application or operation the initial condⁿ of the flipflop should be known. That can be set with the help of the two buttons


⇒ $\text{Preset} = 0$ It sets the ff
 $\text{Clear} = 1$

when $\text{Pr} = 1$ it resets the ff
 $\text{Cr} = 0$

$\text{Pr} = \text{Cr} = 0$ uncertain
 $\text{Pr} = \text{Cr} = 1$ normal ff

Clock

Periodic train of pulses

 

Level triggering
+ve -ve

Edge triggering
+ve -ve


Race around condition (JK ff)

$$S = R$$

When clock pulse of width t_p is applied an i/p $J = K = 1$ with $Q_n = 0$ is applied then after time interval Δt we get o/p $Q = 1$. Now again after time period of Δt we get $Q = 0$. So for whole t_p , o/p keeps on oscillating b/w 0 & 1 and this condⁿ is k/a race around condⁿ.


To overcome this problem there are 2 methods:

- $t_p < \Delta t$
- Master Slave JK ff

 

The master slave ff is made up of 2 JK ff connected in serial manner. Both are collected with clock. Master is one which is driven by +ve clock & slave is driven by -ve

Priority Encoder

 

D_0	D_1	D_2	D_3	Y_1	Y_0
1	0	0	0	0	0
*	1	0	0	0	1
*	*	1	0	1	0
0	0	0	1	1	1

It is giving priority to highest order valid bit

Excitation Table of Flipflop

Sometimes we know the present state & the desired next state. We just have to find what i/p should be given to the ff which can give the desired o/p.

The tabulation of all these cond's is called excitation table of ff


P.S.	N.S.	S	R	
0	1	1	0	
0	0	0	x	SR
1	1	x	0	
1	0	0	1	

PS	NS	J	K	
0	1	1	x	JK
0	0	0	x	
1	1	x	0	
1	0	x	1	

PS	NS	T
0	0	0
0	1	1
1	0	1
1	1	0

PS	NS	D
0	0	0
0	1	1
1	0	0
1	1	1

 Conversion from one flipflop to another flipflop



To design a conversion logic we need to combine the excitation table of both FF then make the truth table with data i/p & Q as i/p and i/p of given ff as o/p.

Q. Make D flipflop using SR ff.

D	Q_n	Q_{n+1}	S	R
0	0	0	0	x
0	1	0	0	1
1	0	1	1	0
1	1	1	x	0

Q_n	D	
0	0	1
0	1	
1	0	x
1	1	

$$S = D$$

Q_n	D	
0	0	x
0	1	
1	0	1
1	1	

$$R = \bar{D}$$

Counter Designing

MOD-7 It can count 7 different stages

JK FF or T FF to design counter

$$\text{No. of FF} = 2^n \quad \text{No. of stages} = 2^n - 1$$

PS NS

0	1
1	2
2	3
3	4
4	5
5	0

PS NS

000	001
001	010
010	011
011	100
100	101
101	000

~~##~~

Design Mod-3 counter with JK FF

PS	NS	J ₁ K ₁	J ₀ K ₀
00	01	0 x	1 x
01	10	1 x	x 1
10	00	x 1	0 x

	q_0		J_1
	0	1	
q_1			
0		1	
1	X	X	

$$J_1 = q_0$$


$$K_1 = 1$$

	q_0		K_1
	0	1	
q_1			
0	X	X	
1	1	X	

$$J_0 = \bar{q}_0$$

$$K_0 = 1$$

Draw ckt diagram

 

lockout condⁿ

Sometimes during working of the counter it goes into some unused state & keeps on counting those unused states and never come back to the demanding state is called lockout condⁿ.

To overcome this problem there are 2 methods.

- ① Self starting counters
- ② Self correcting counters

Finite State Machines

As we know sequential m/c's are those in which o/p is a fn of i/p, past i/p's & o/p's & internal states of flipflop.

A finite state m/c is an abstract model of sequential m/c's b'coz they have a limited state capacity with fixed no. of states that are actually used in the calculation of o/p depend on i/p conditions.

There are two models of finite state m/c's:

- i) Mealy type model
- ii) Moore type model

In Mealy models we are considering that o/p is a fn of present state & present i/p whereas in Moore mode o/p is a fn of present state only.

→ State diagrams

The state diagram is a pictorial representation of the relationship b/w present state i/p, next state and o/p of the sequential ckt.


→ State Table

The state table is tabular representation in tabular form of i/p, o/p, present state & next state.

Suppose a sequential ckt has four states A, B, C, D


PS	NS, o/p	
	I/p x	
	x=0	x=1
A	A, 0	B, 0
B	B, 1	C, 0
C	D, 0	C, 1
D	D, 0	A, 1

Melay

 

For Moore diagram
The state

PS	NS			o/p
	x=0	I/p x	x=1	
a	a		b	0
b	b		c	0
c	d		c	1
d	a		d	0

 

State Reduction

→ State Assignment

The assignment of binary values to the is called state assignment.

→ Transition and o/p Table:

PS	N.S.		o/p	
	x=0	x=1	x=0	x=1
a	a	b	0	0

When you are separating the column for & o/p for the state table, the table is k/ transition & o/p table.

Minimization of completely specified sequential m/c using partition technique

PS	NS, Z	
	x = 0	x = 1
A	C, 0	F, 0
B	D, 1	F, 0
C	E, 0	B, 0
D	B, 1	E, 0
E	D, 0	B, 0
F	D, 1	B, 0

Step 1:

$$P_1 = (A, C, E) (B, D, F) \\ (C, E, D) (D, B, D) \quad 0 \text{ successor}$$

$$(A, C, E) (B, D, F) \\ (F, B, B) (F, E, B) \quad 1 \text{ successor}$$

$$P_2 = (A, C) (E) (B, F) (D)$$

$$0 \Rightarrow (C, E) (D) (D, D) (B)$$

$$1 \Rightarrow (F, B) (B) (F, B) (E)$$

$$P_3 = (A) (C) (E) (B, F) (D)$$

$$0 \Rightarrow (C) (E) (D) (D, D) (B)$$

$$1 \Rightarrow (F) (B) (B) (F, B) (E)$$

$$P_3 = (A) (C) (E) (B, F) (D)$$

$\Rightarrow B$ & F are equivalent

For the table given below

P.S	NS, Z	
	X=0	X=1
A	F, 0	B, 0
B	D, 0	C, 0
C	F, 0	E, 0
D	G, 1	A, 0
E	D, 0	C, 0
F	F, 1	B, 1
G	G, 0	H, 0
H	G, 1	A, 0

$$P_1 = (A, B, C, E, \cancel{F}, G) (D, H) (F)$$

$$0 \Rightarrow (F, D, \underset{x}{F}, D, G) (G, G) (F)$$

$$1 \Rightarrow (B, C, \underset{x}{E}, C, H) (A, A) (B)$$

$$P_2 = (\cancel{A}, C) (B, E) (G) (D, H) (A, C) (B, E) (G) (D, H) (F)$$

$$0 \Rightarrow (F, F) (D, D) (G) (G, G) (F)$$

$$1 \Rightarrow (B, E) (C, C) (H) (A, A) (B)$$

$$A \equiv C \quad B \equiv E \quad D \equiv H$$